

Generator coil Tests

V1.1

2021-01-06

Content:

Generator Coil Tests *No coil shortening / No loads*

Test 1.xx Open Coil

Test 2.xx Cap + Diode

Test 3.xx 2x Cap + 2x Diode

Conclusion Tests 1.xx/2.xx/3.xx

Generator Coil Tests *Coil shortening / No loads*

Test 4.02 2 mm gap - 2x Cap + 2x Diode + Reed Switch

Test 4.20 20 mm gap - 2x Cap + 2x Diode + Reed Switch

Test 5.20 20 mm gap - 2x Cap + 2x Diode + 2x Reed Switch

Test 6.20 20 mm gap - 2x Cap + 2x Diode + Hall + MOSFET

Conclusion Tests 4.xx/5.xx/6.xx

Appendix 1: Hall sensor circuit verification

Appendix 2: Original Test 6.20 – 20 mm gap

Appendix 3: Parameters for Tests



Appendix 4: Trigger Coil Test

Generator coil Tests




1.xx/2.xx/3.xx

No coil shortening / No loads




- Coil wire AWG 16
- 4x Coil 291 windings, in series
- Total 1164 windings
- Total inductance +/-1.35H
- Core = welding rods, DIN 8554:G1 (=R45)

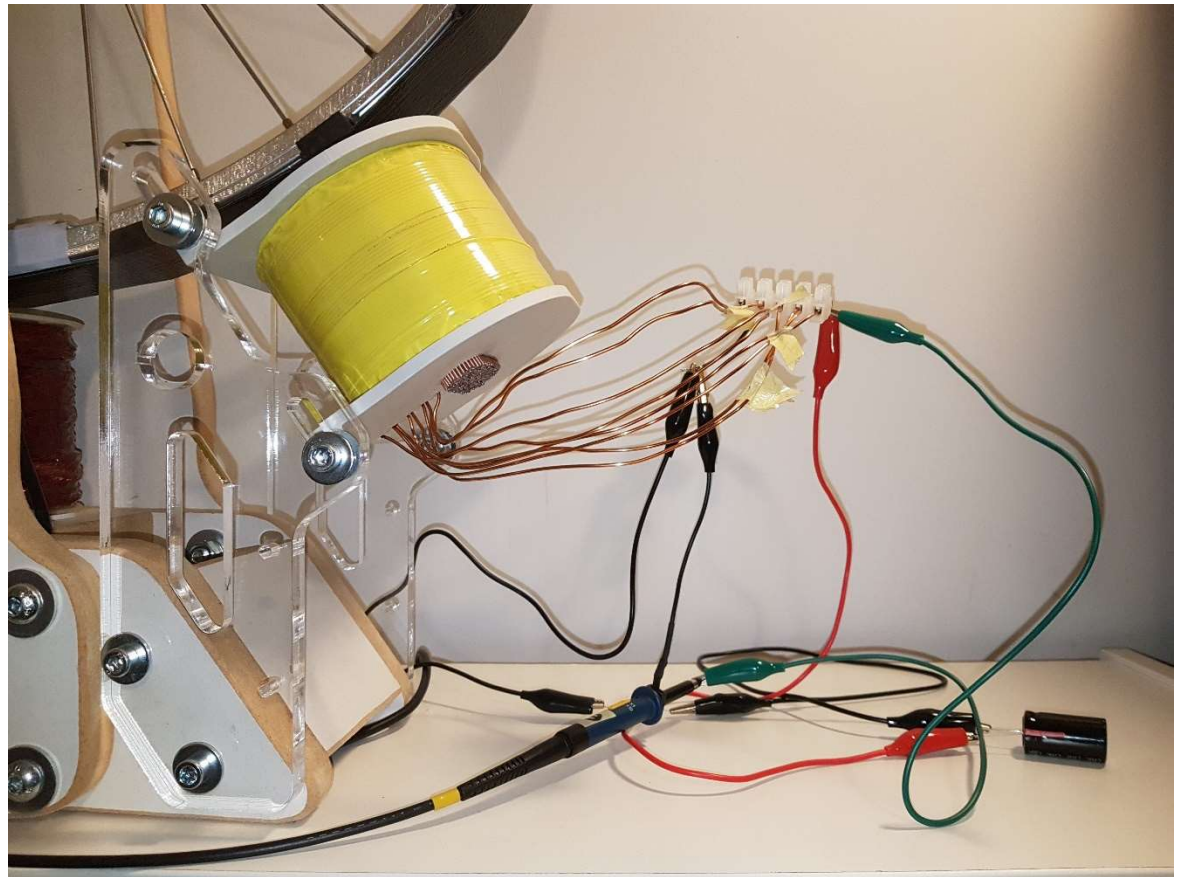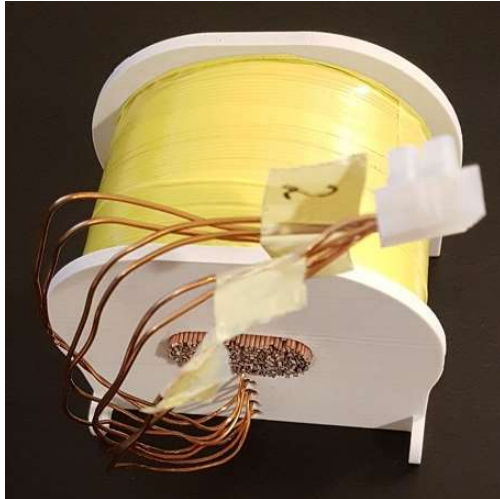

Test 1.xx Open Coil

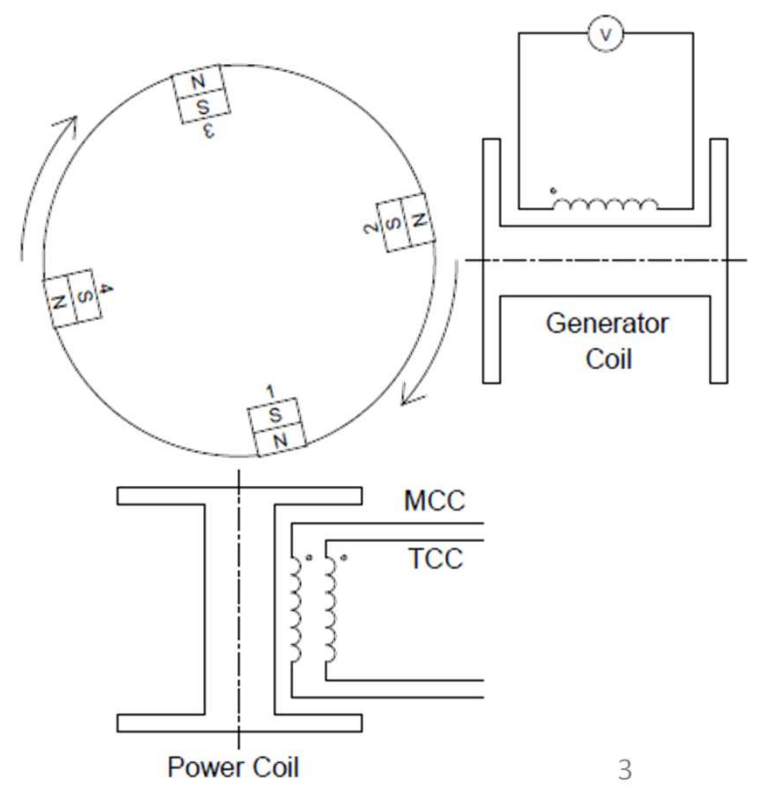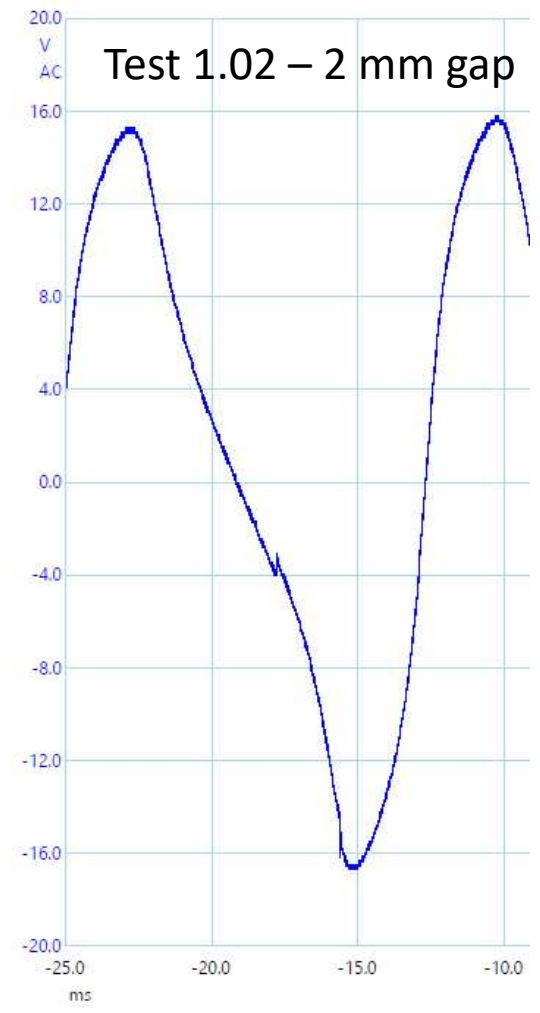
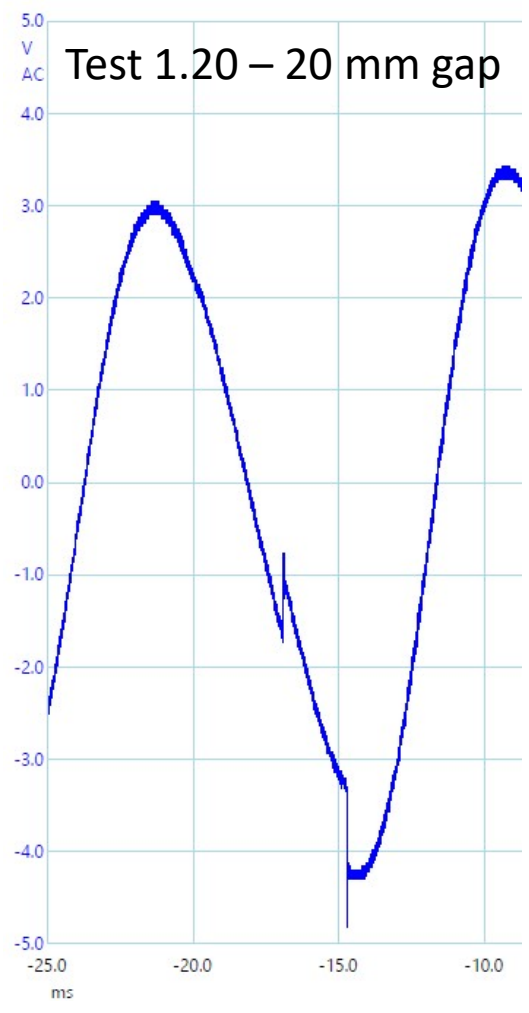


Test 2.xx Cap + Diode

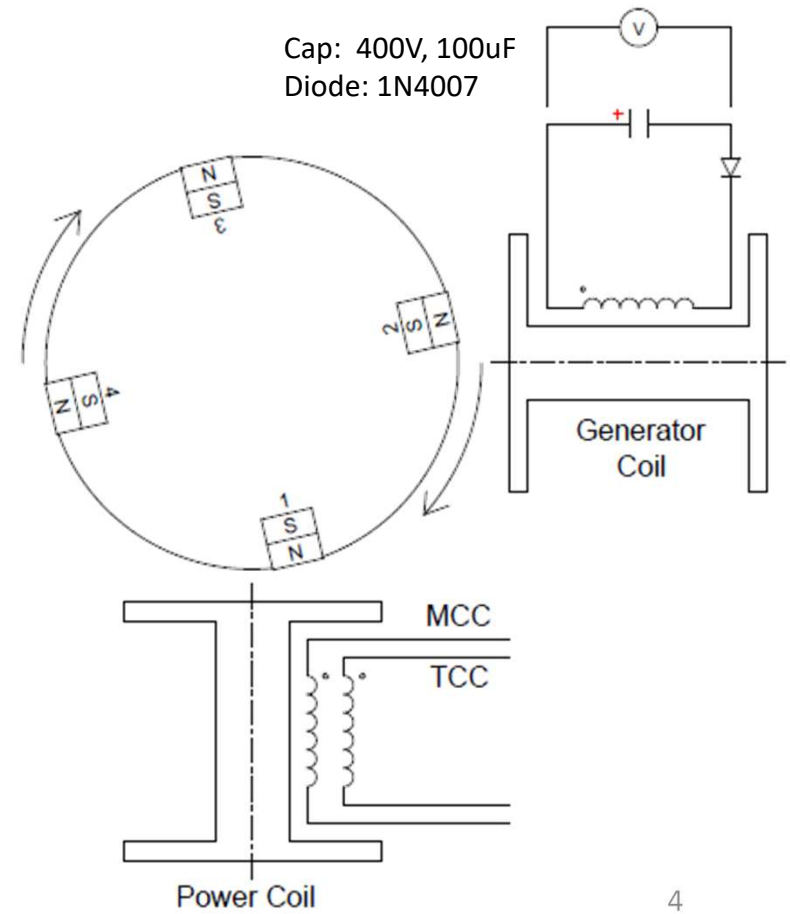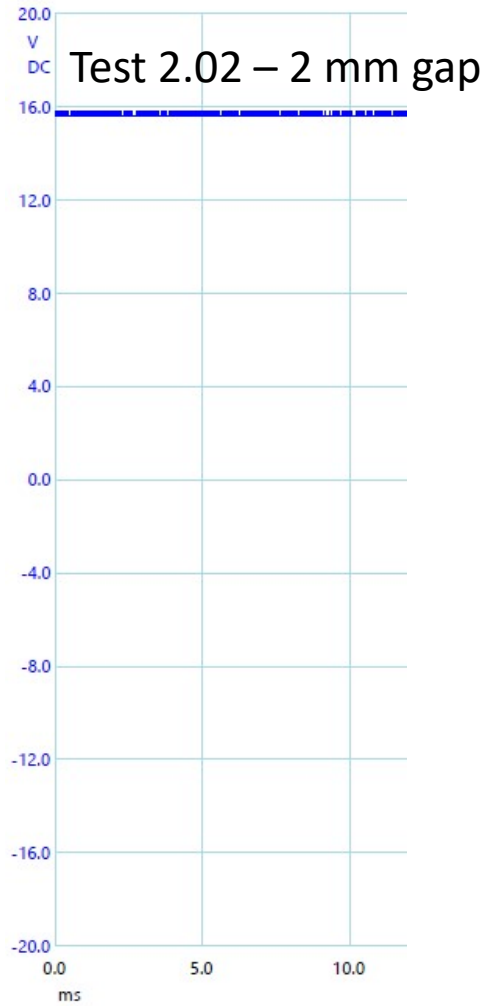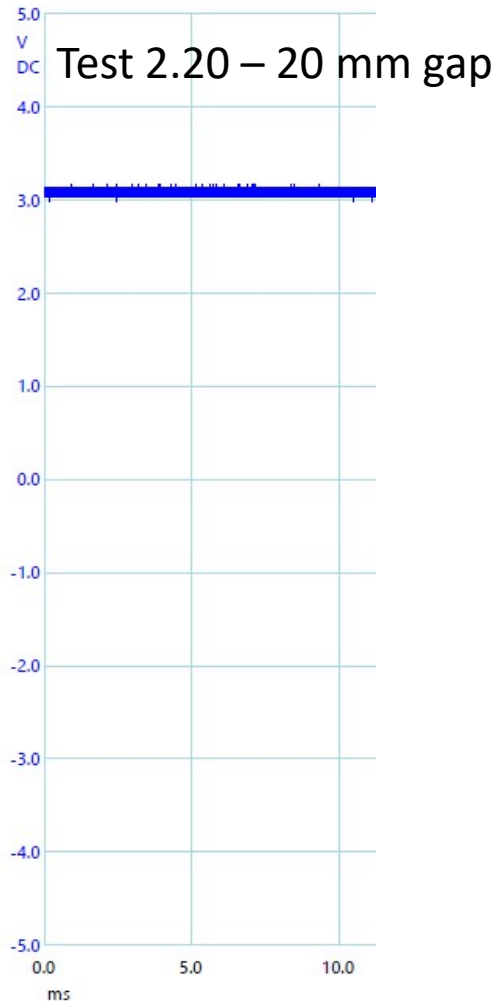

Test 3.xx

2x Cap + 2x Diode

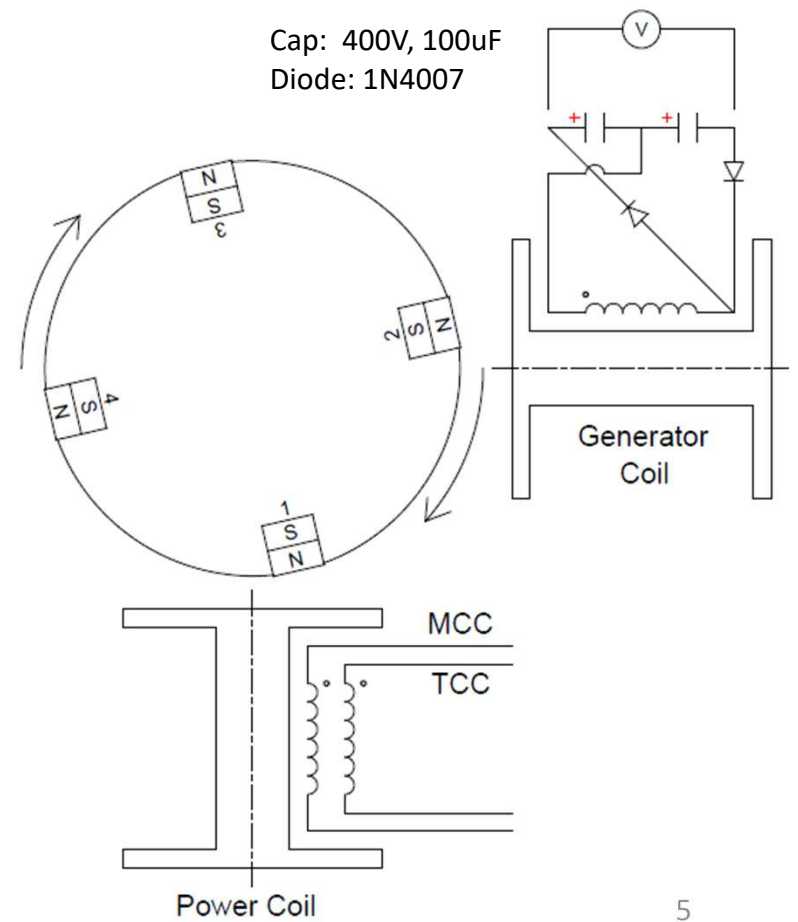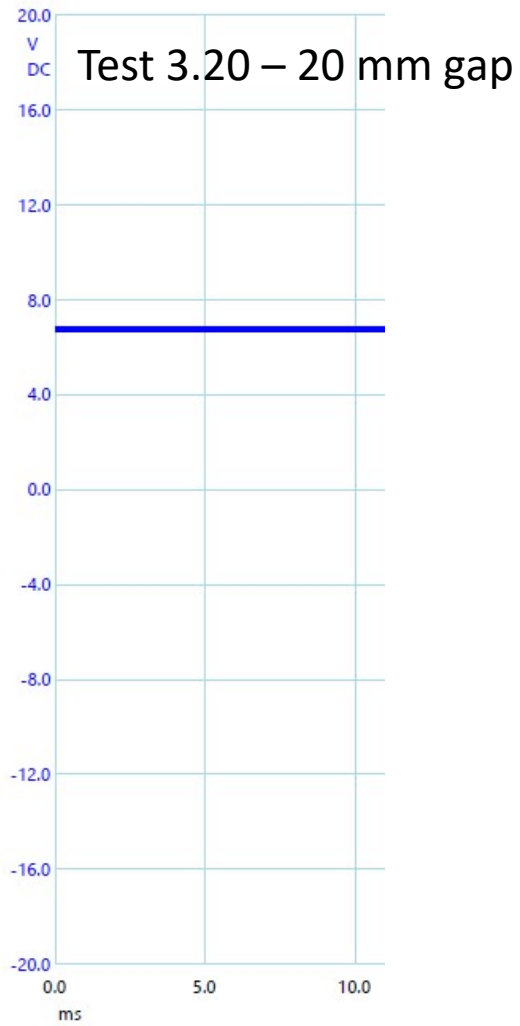

Conclusion Tests 1.xx/2.xx/3.xx: No coil shortening / No loads



-The setup of test 3.xx yielded the highest voltage in the capacitors

-When the coil is closer to rotor, induced voltage increases, but causes more drag on the rotor too; rpms drop. However, to see the clear effect of this, a full charge cycle should be done with each setup. Now it was just a couple of minutes with each setup. So at every test the output battery was a bit more charged which increased the rpm (and decreases the amps) too.

Generator coil Tests




4.xx/5.xx/6.xx
Coil shortening / No loads

- Coil wire AWG 16
- 4x Coil 291 windings, in series
- Total 1164 windings
- Total inductance +/-1.35H
- Core = welding rods, DIN 8554:G1 (=R45)

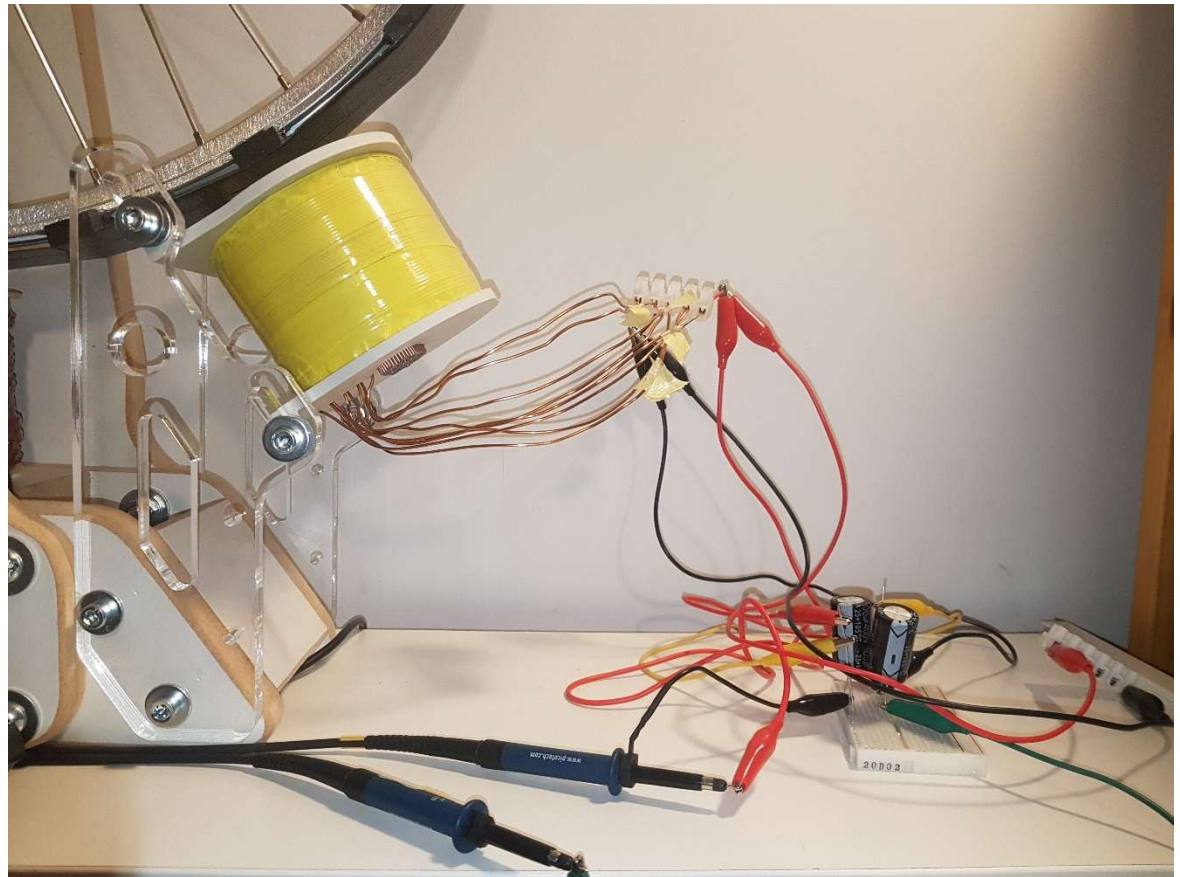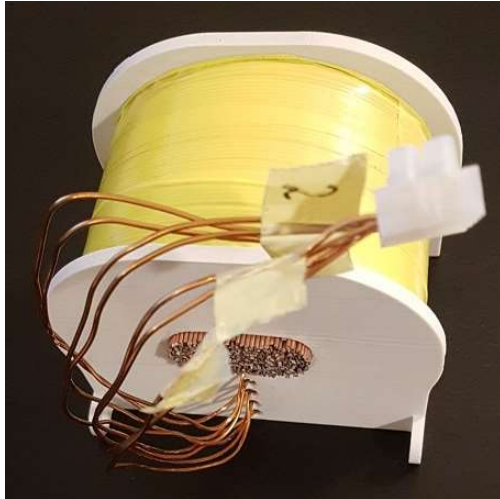




Test 4.02

2 mm gap - 2x Cap + 2x Diode + Reed Switch

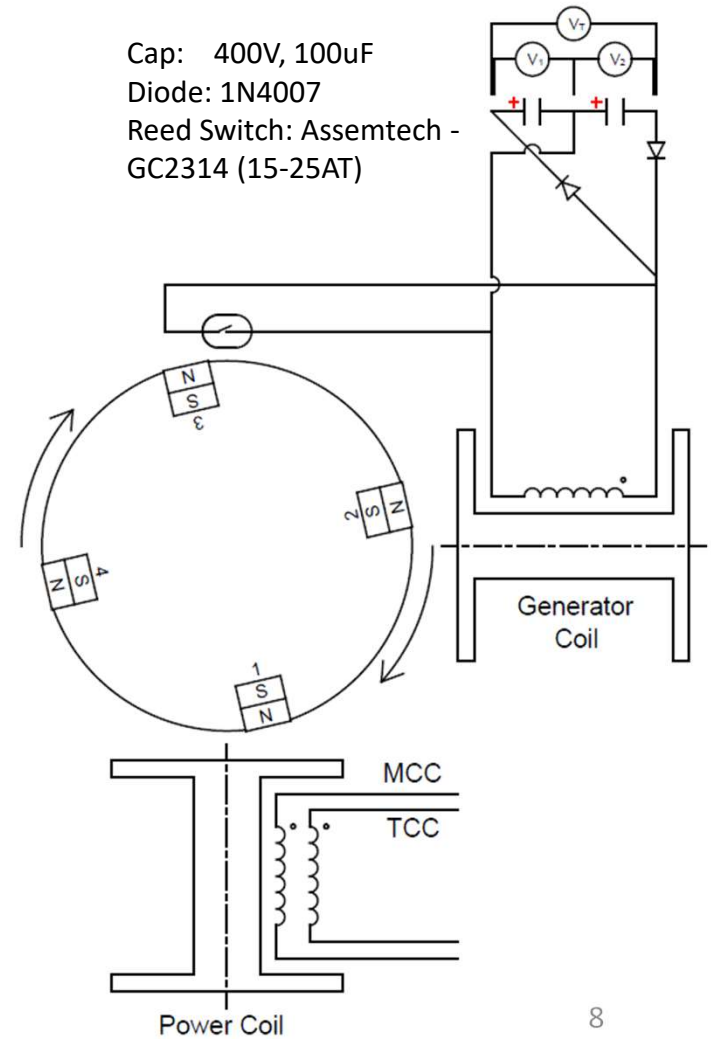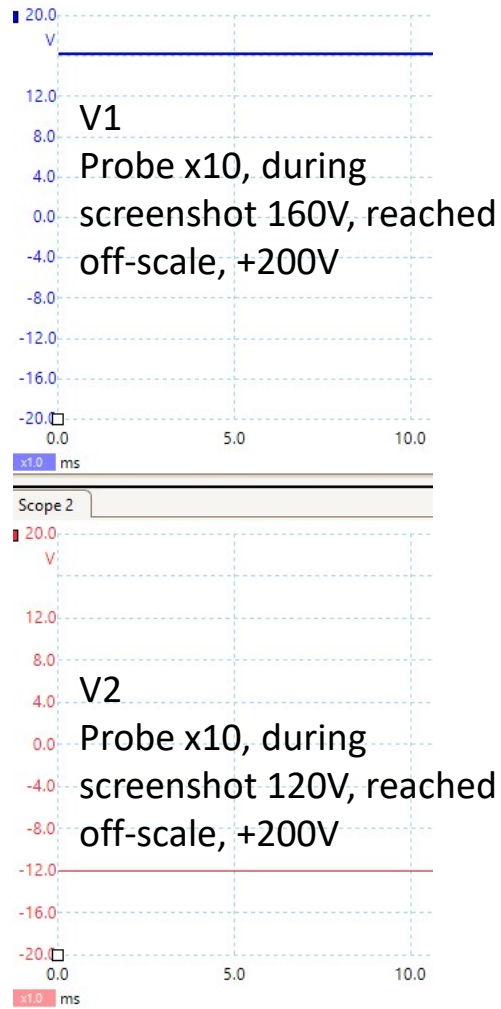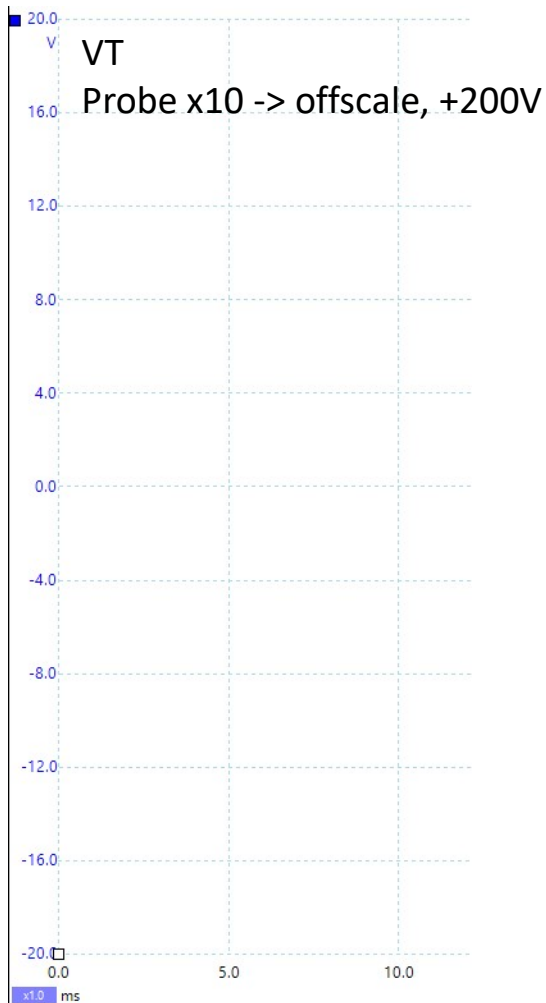

Test 4.20

20 mm gap - 2x Cap + 2x Diode + Reed Switch

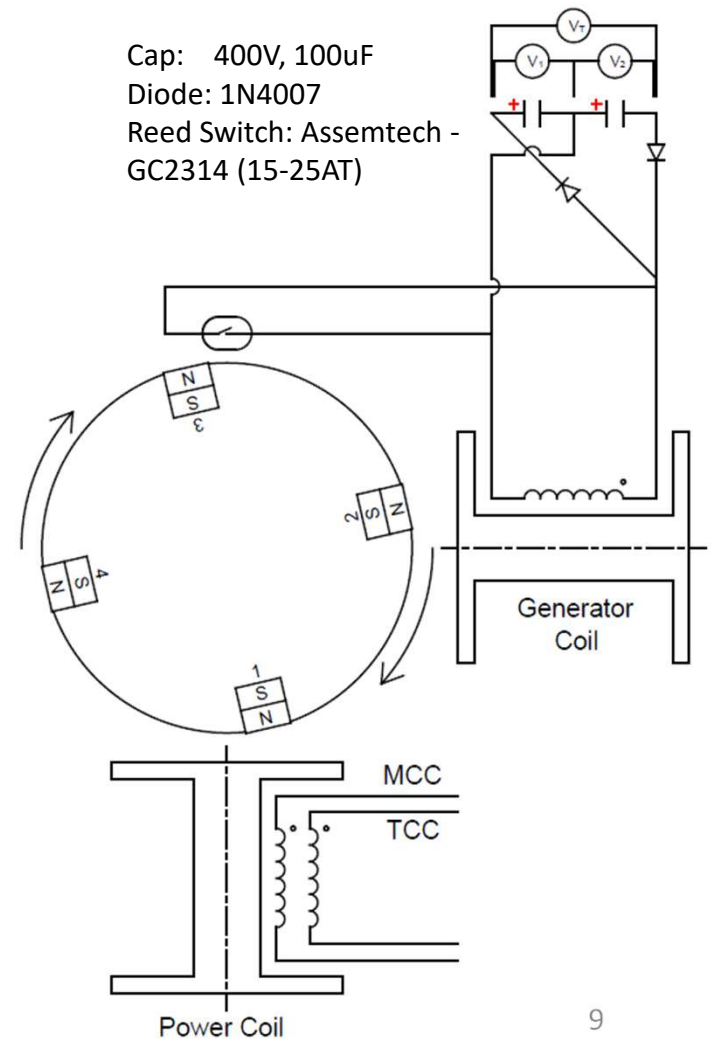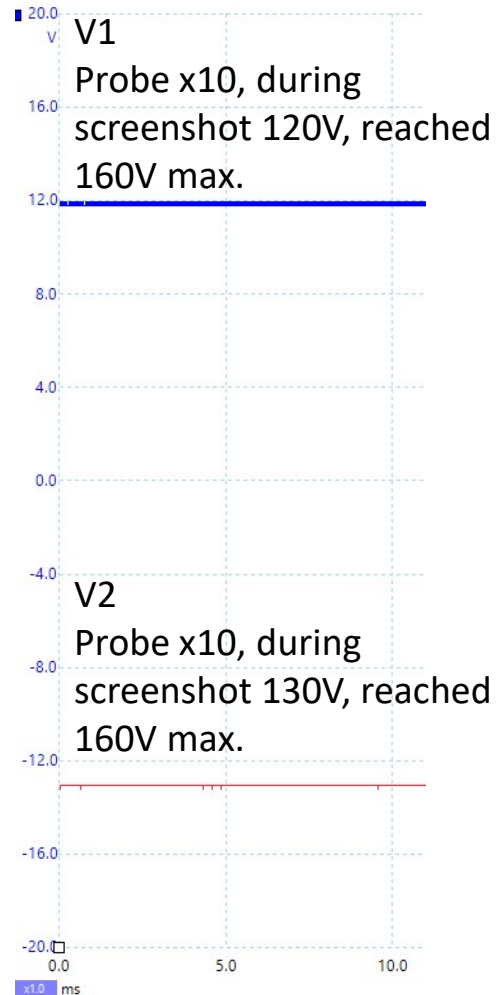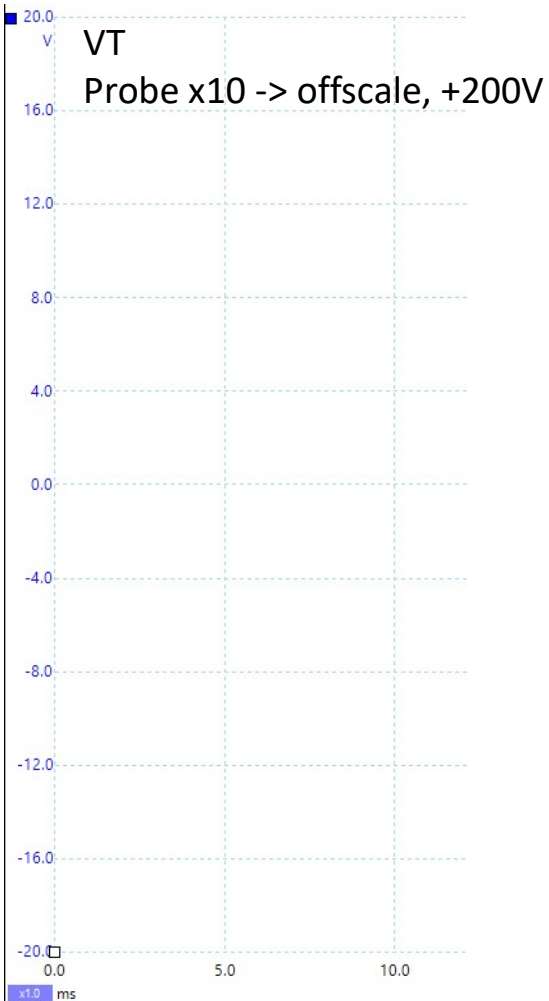

Test 5.20



20 mm gap - 2x Cap + 2x Diode + 2x Reed Switch

Explanation

When monitoring the voltage of the caps individually with two probes in test 4.xx, it showed that the position of the reed switch determined which of the two caps was charging fastest. At some position they both seemed to charge, but not as fast if the reed switch was slightly moved and only one cap was charging. I tried to experiment with two reed switches to see if this would make a difference.

Conclusion:




Two Reed switches did not seem to make a difference. However, all of these observations are a bit uncertain since at the same time I was trying to maintain the reed switch(es) at the same position (or varying) while looking at my scope at the same time. For a better result/conclusion these experiments should be done again with adjustable fixed positions of the reed switches.

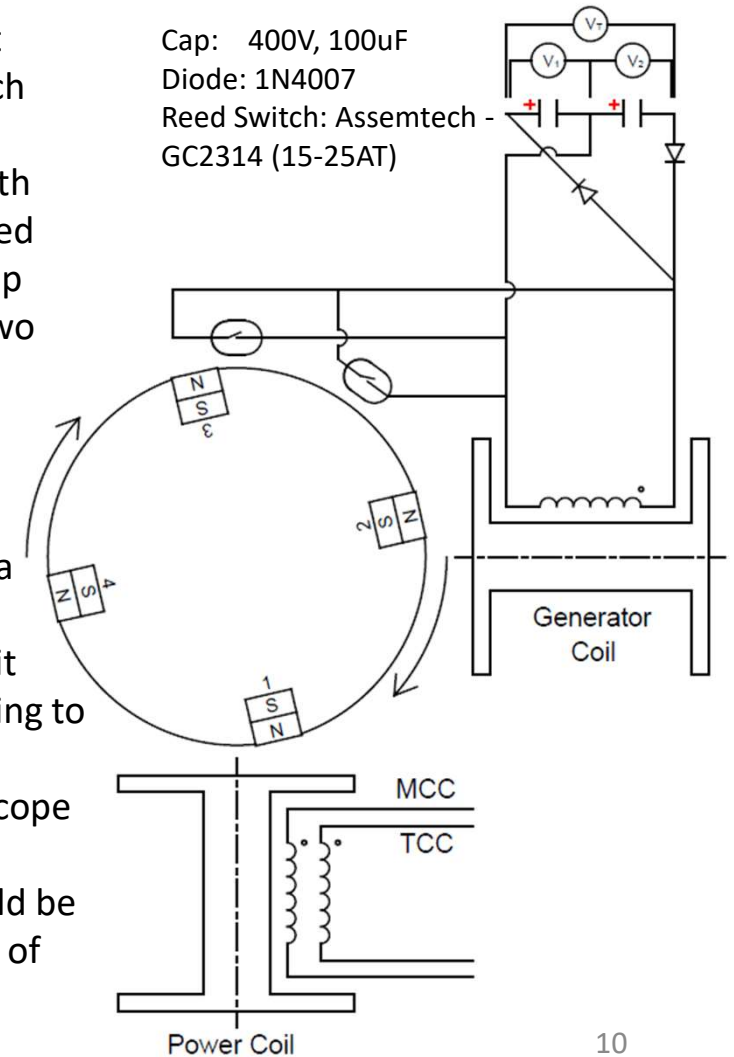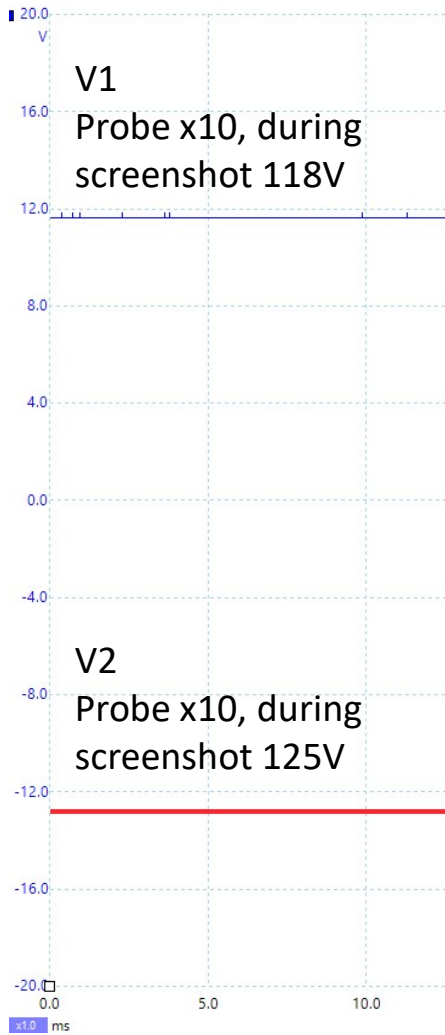

Test 6.20

Conclusion: 20 mm gap - 2x Cap + 2x Diode + Hall + MOSFET

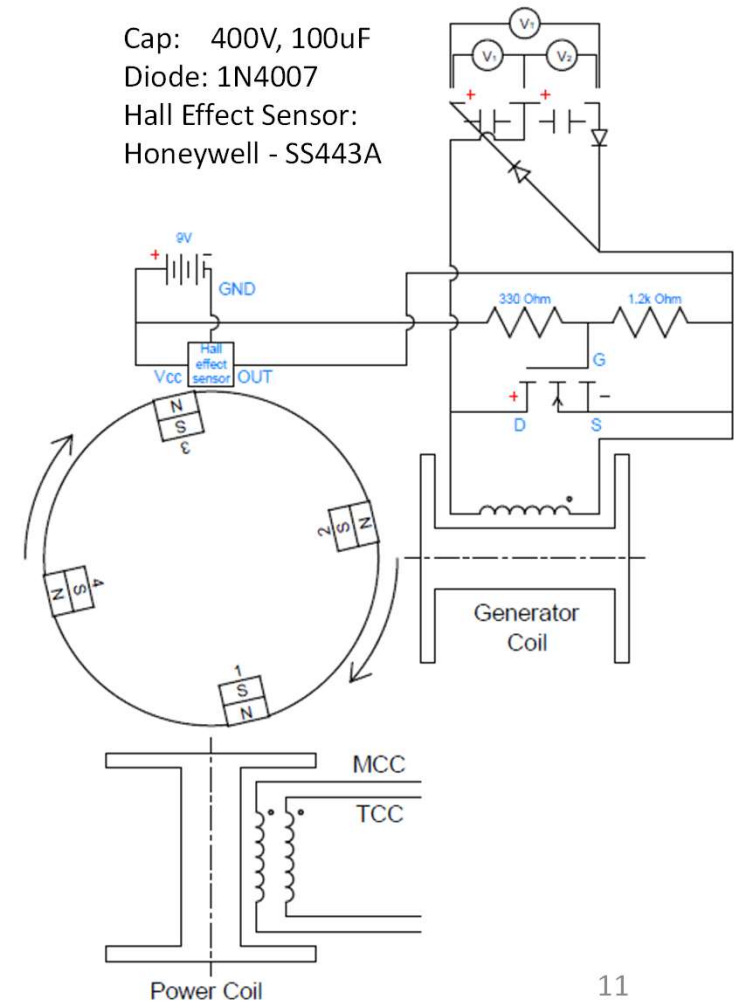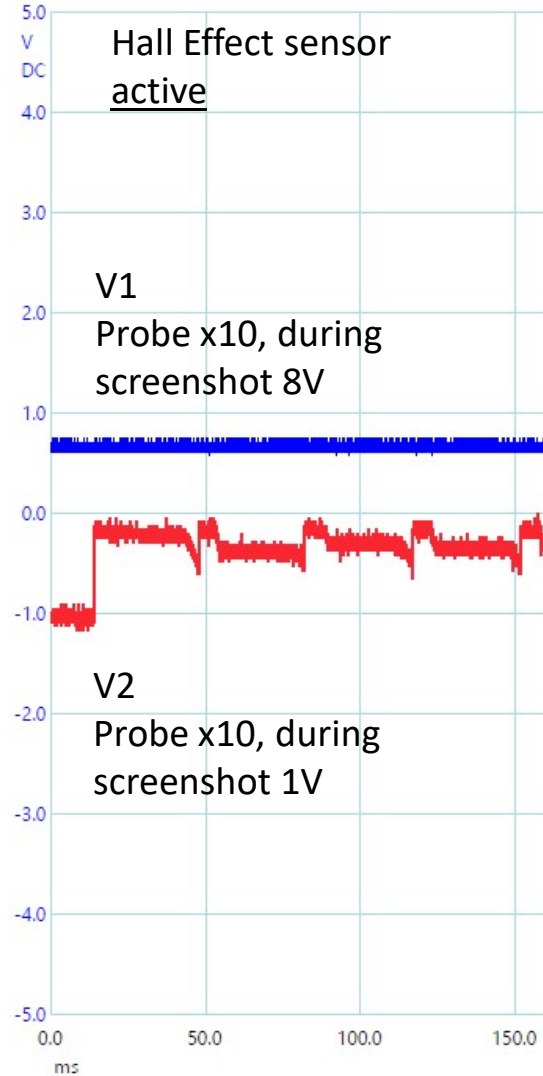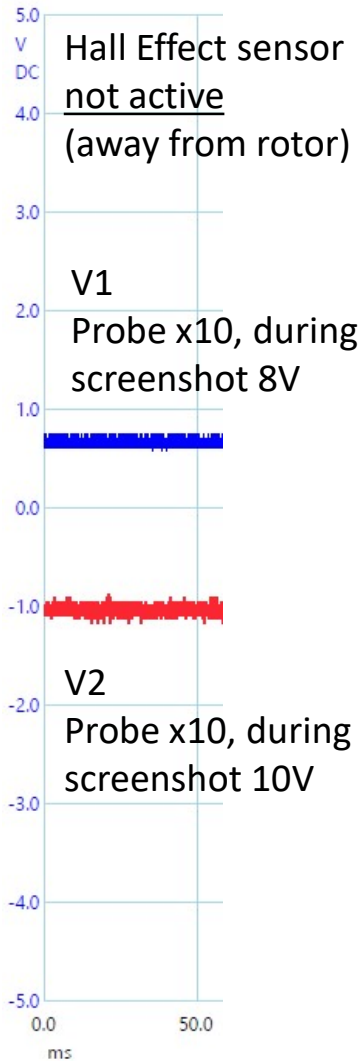The coil-shortening with the hall effect sensor seemed to have a reverse effect: with the hall active the voltage in the capacitor with V2 dropped. It might be due to that my circuit as depicted below is not correct. Furthermore the capacitor with V1 seemed to be unaffected. For more information see Appendix 1 & 2.



Conclusion Tests 4.xx/5.xx/6.xx: coil shortening / No loads

General

When the coil is closer to rotor, induced voltage increases, but causes more drag on the rotor too; rpms drop. However, to see the clear effect of this, a full charge cycle should be done with each setup. Now it was just a couple of minutes test with each setup. So at every test the output battery was a bit more charged which increased the rpm (and decreases the amps) too.

Reed Switch

Coil shortening with the Reed Switch has a significant effect on the voltage in the capacitors. For the max. effect of this coils shortening the position of the reed switch is very specific/sensitive.

Although the Reed Switch yielded excellent preliminary results, it is a tiny mechanical switch which is likely to fail at some point.

Hall Effect Sensor

Coil shortening with the Hall Effect Sensor so far has not yielded good results. One of the main reasons for this is probably due to the fact that my Hall effect sensor only responded to one side of the magnetic field of the magnets, while the Reed Switch responded to both.


Further more my circuit design for the Hall Sensor might be incorrect.

Next tests/steps:

- Make an adjustable fixed bracket for the reed switch Sensor to optimize/further investigate max effect.
- Ask for input on Hall effect sensor circuit/redesign/investigate. Or consider replacing hallsensor with (trigger) coil
- Setup new tests with loads (LEDs & resistors)


Appendix 1.1

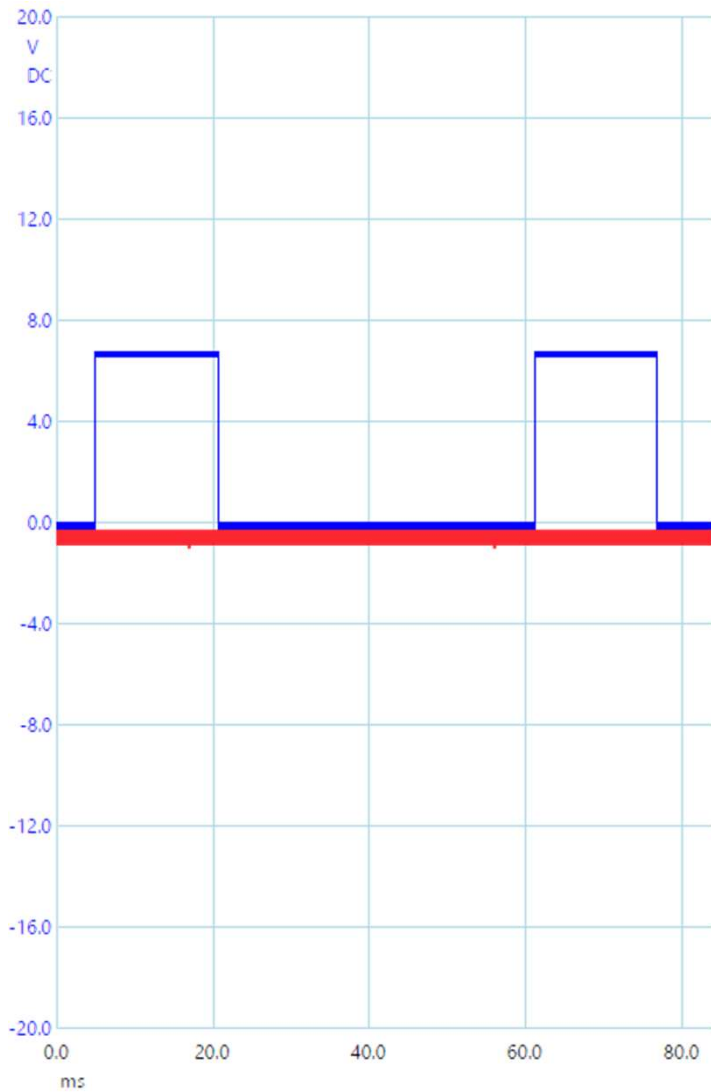Hall sensor circuit verification Test 6.20 – Hall sensor verification




Note:

-Scope Connected as indicated, blue trace (ignore red trace)

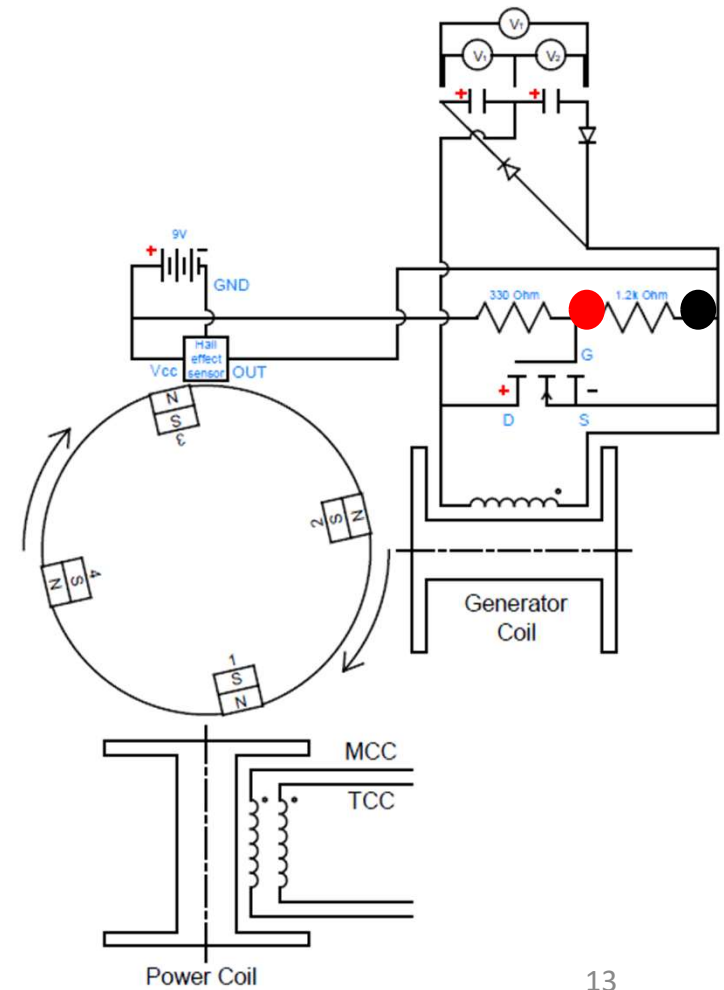


Appendix 1.2

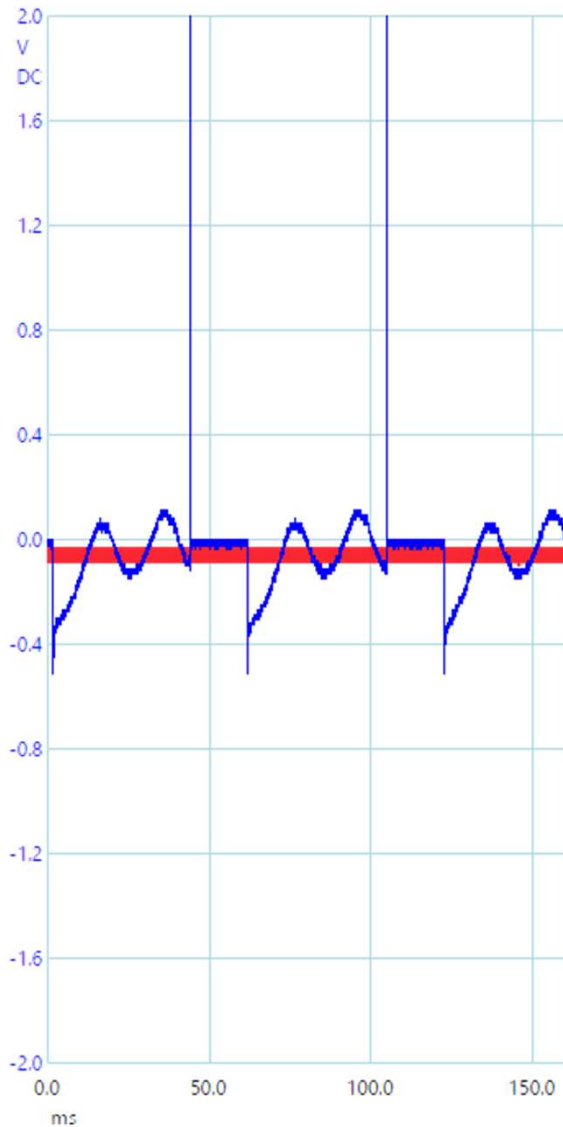Hall sensor circuit verification Test 6.20 – MOSFET verification




Note:

- Scope Connected as indicated, blue trace (ignore red trace)
- Mind that DRAIN was not connected

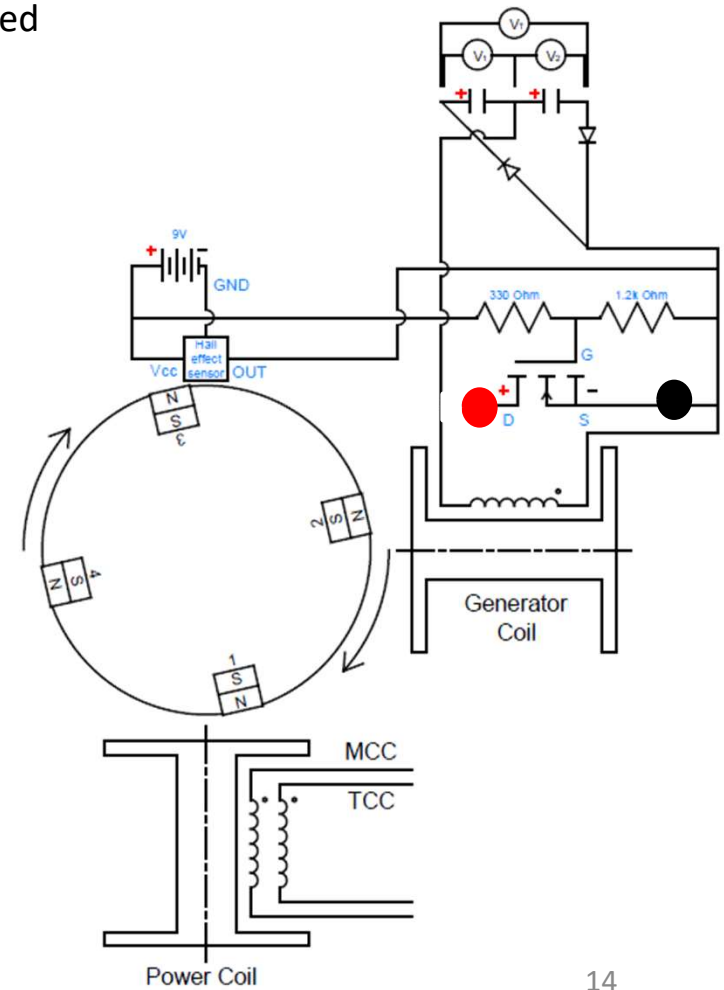


Appendix 1.3

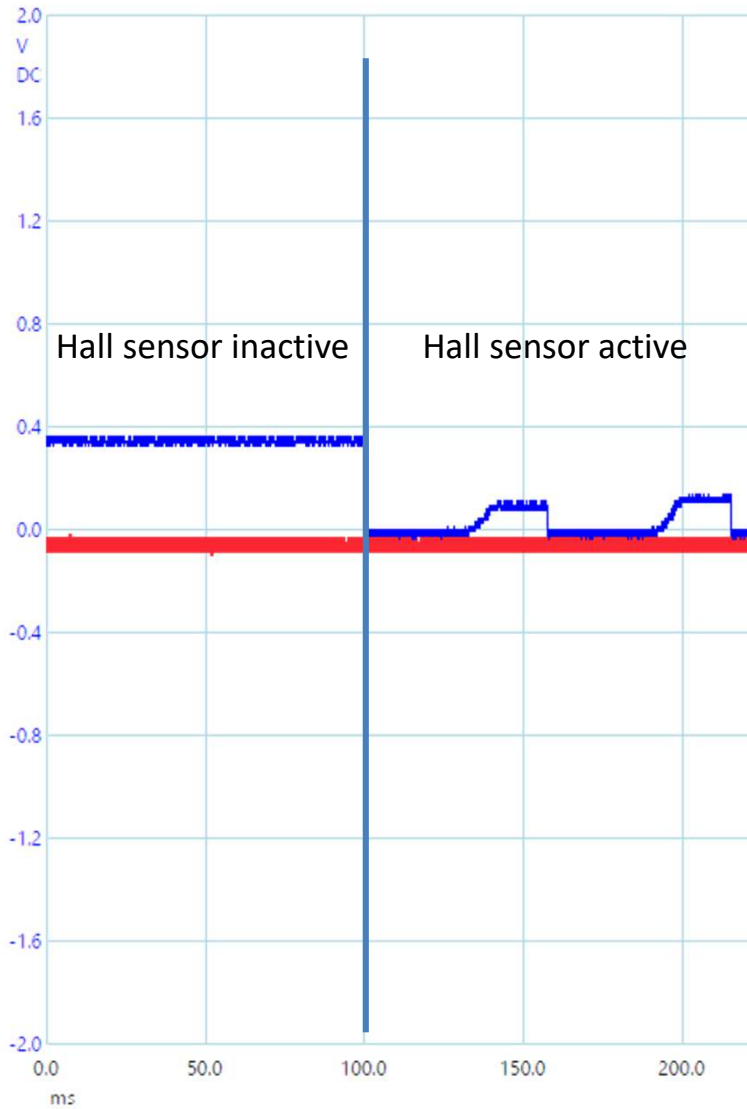Hall sensor circuit verification Test 6.20 – MOSFET verification



Note:

-Scope Connected as indicated, blue trace (ignore red trace)

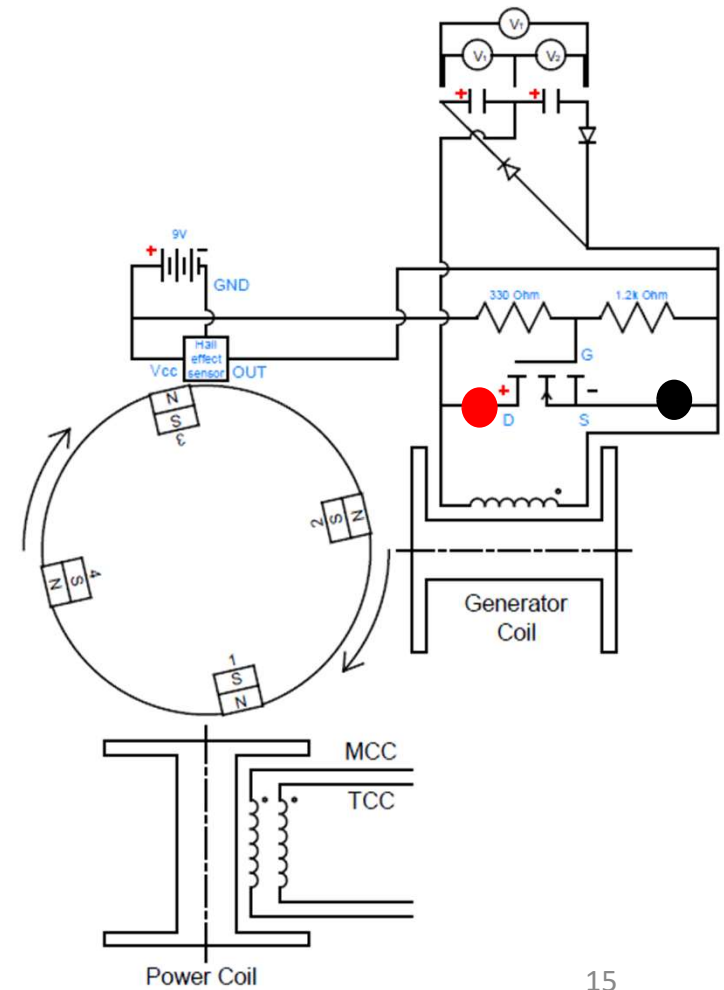

Appendix 2

Original Test 6.20 – 20 mm gap





Conclusion:

Same conclusion as Test 6.20

Note:

Difference in circuit comp. to Test 6.20:

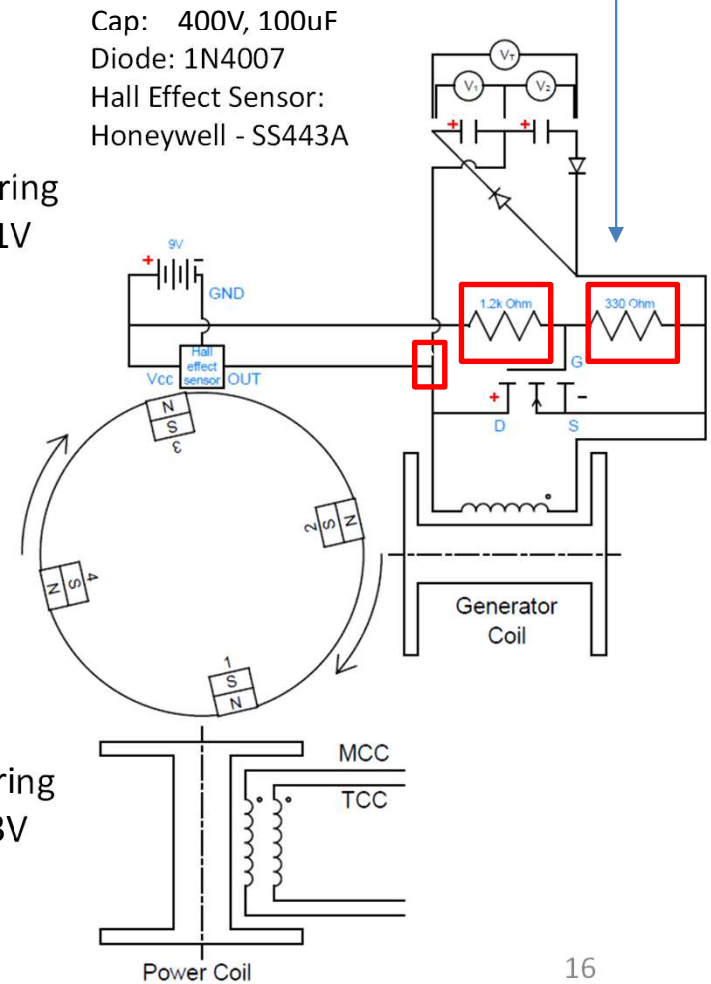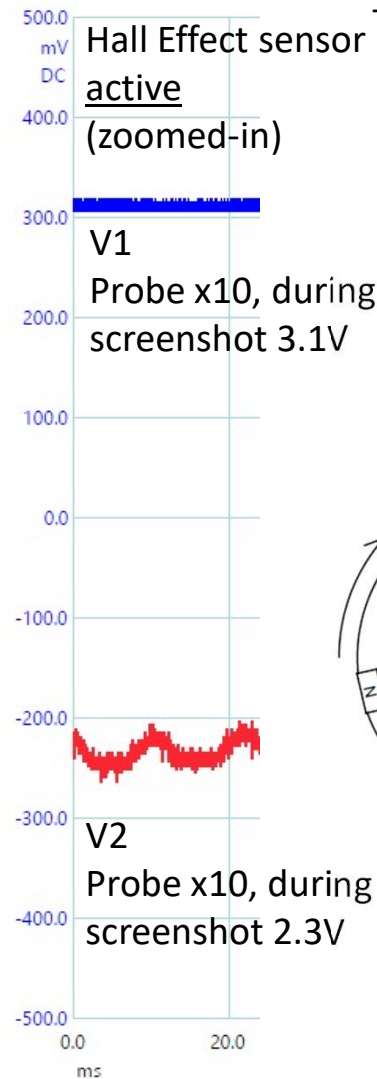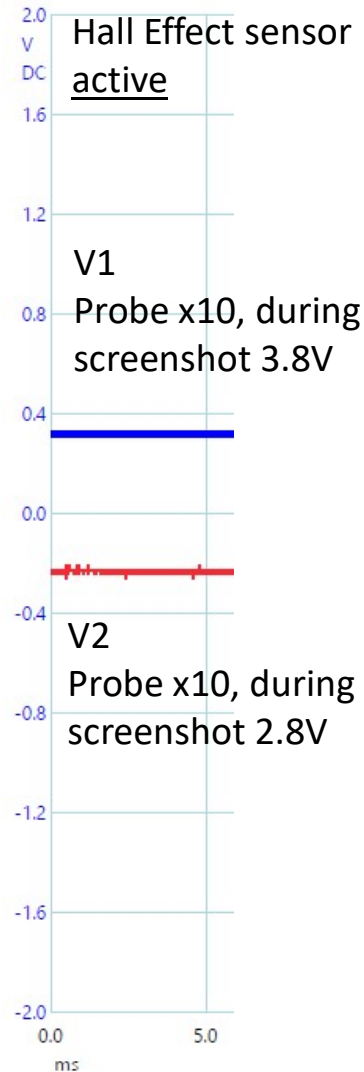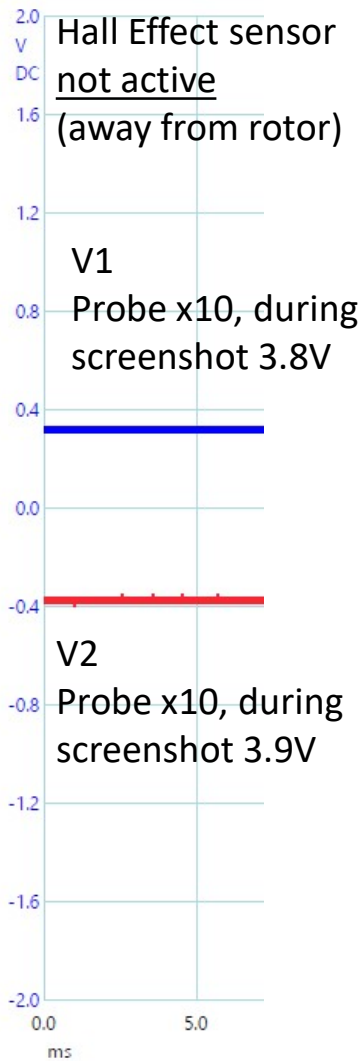- Resistors swapped (incorrect)
- Output of Hall connected differently




Appendix 3 Parameters for Tests

		Gen coil gap 20mm	Gen coil gap 2mm	Gen coil gap 2mm	Gen coil gap 20mm	Gen coil gap 20mm	Gen coil gap 2mm
Cycle	-	GEN 1.20	GEN 1.02	GEN 2.02	GEN 2.20	GEN 3.20	GEN 3.02
Date	-	2020-12-29	2020-12-29	2020-12-29	2020-12-29	2020-12-29	2020-12-29
Rotor magnets, amount/width	-/mm	21 / 22mm	21 / 22mm	21 / 22mm	21 / 22mm	21 / 22mm	21 / 22mm
Gap	mm	8	8	8	8	8	8
Mode	-	CG	CG	CG	CG	CG	CG
Power coils	-	8	8	8	8	8	8
Flywheel weight	kg	N/A	N/A	N/A	N/A	N/A	N/A
Output battery	ID-type	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)
Output voltage @ rest, before/after testing	V	12.49 / ??	12.64 / ??	12.66 / ??	12.79 / ??	12.67 / ??	12.79 / ??
Input battery 1	ID-type	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)
Input voltage 1 @ rest, before/after testing	V	12.51 / ??	12.48 / ??	12.48 / ??	12.44 / ??	12.47 / ??	12.42 / ??
Input battery 2	ID-type	N/A	N/A	N/A	N/A	N/A	N/A
Input voltage 2 @ rest, before/after testing	V	N/A	N/A	N/A	N/A	N/A	N/A
Input parallel voltage (bat 1 + bat 2)	V	N/A	N/A	N/A	N/A	N/A	N/A
Input voltage @ start running	V	12.13	12.16	12.16	12.13	12.12	12.12
Input voltage @ end running	V	??	??	??	??	??	??
Amp @ start	A	2	1.8	1.75*	1.82	1.9	1.78
Amp @ end	A	??	??	??	??	??	??
RPM @ start/end	rpm	244 / ??	231 / ??	231 / ??	259 / ??	260 / ??	243 / ??
Time to charge to 15.3V	min	??	??	??	??	??	??
Ah to charge to 15.3V	Ah	#VALUE!	#VALUE!	#VALUE!	#VALUE!	#VALUE!	#VALUE!
COP	-	#VALUE!	#VALUE!	#VALUE!	#VALUE!	#VALUE!	#VALUE!
Variable resistance	Ohm	62.2	62.2	62.2	62.2	62.2	62.2



		Gen coil gap 2mm	Gen coil gap 20mm	Gen coil gap 20mm	Gen coil gap 20mm
Cycle	-	GEN 4.02	GEN 4.20	GEN 5.20	GEN 6.20
Date	-	2021-01-02	2021-01-02	2021-01-02	2021-01-05
Rotor magnets, amount/width	-/mm	21 / 22mm	21 / 22mm	21 / 22mm	21 / 22mm
Gap	mm	8	8	8	8
Mode	-	CG	CG	CG	CG
Power coils	-	8	8	8	8
Flywheel weight	kg	N/A	N/A	N/A	N/A
Output battery	ID-type	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)	X1 (AGM/12Ah)
Output voltage @ rest, before/after testing	V	12.51 / ??	12.80 / ??	12.49 / ??	12.56 / ??
Input battery 1	ID-type	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)	LA1 (Flooded/24Ah)
Input voltage 1 @ rest, before/after testing	V	12.53 / ??	12.45 / ??	12.59 / ??	12.48 / ??
Input battery 2	ID-type	N/A	N/A	N/A	N/A
Input voltage 2 @ rest, before/after testing	V	N/A	N/A	N/A	N/A
Input parallel voltage (bat 1 + bat 2)	V	N/A	N/A	N/A	N/A
Input voltage @ start running	V	12.17	12.11	12.23	12.12
Input voltage @ end running	V	??	??	??	??
Amp @ start	A	1.8	1.82	1.95	1.85
Amp @ end	A	??	??	??	??
RPM @ start/end	rpm	234* / ??	257* / ??	248* / ??	255* / ??
Time to charge to 15.3V	min	??	??	??	??
Ah to charge to 15.3V	Ah	#VALUE!	#VALUE!	#VALUE!	#VALUE!
COP	-	#VALUE!	#VALUE!	#VALUE!	#VALUE!
Variable resistance	Ohm	62.2	62.2	62.2	62.2

Appendix 4.1
Trigger Coil test
No loads
Gap +/-11mm

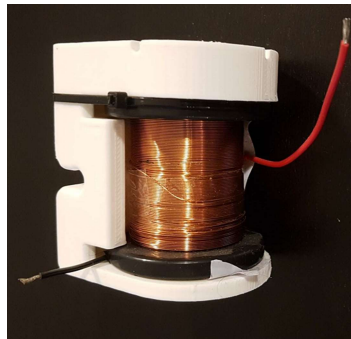*-Coil wire AWG 26
-+/- 732 windings
-Inductance no core +/-0.13H*




*-Inductance with core +/-0.27H
-Core = welding rods, DIN
8554:G1 (=R45)*

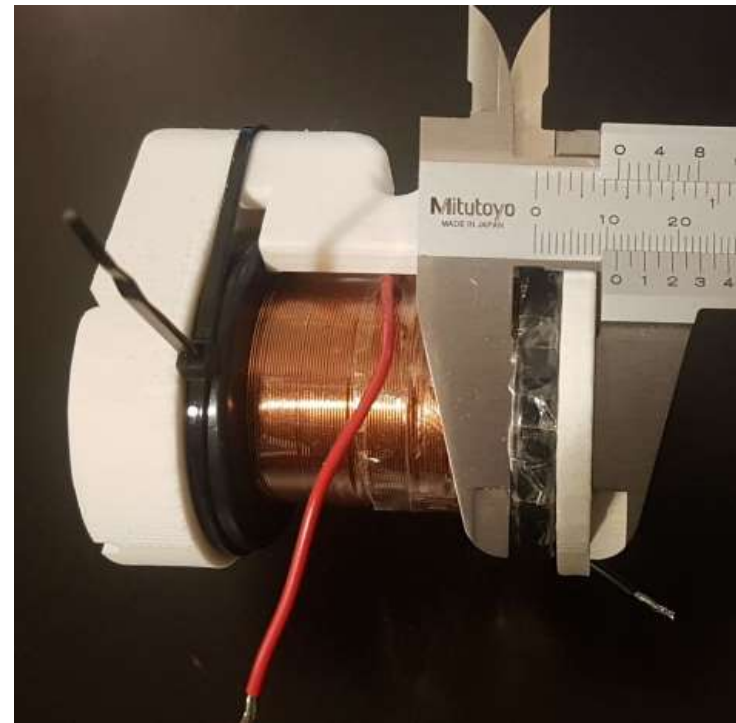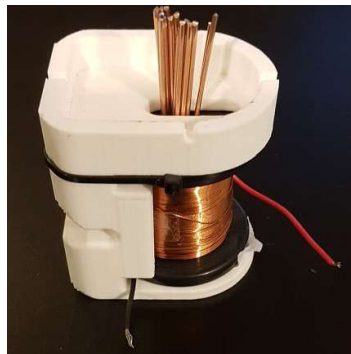

Appendix 4.2 Trigger Coil test

Note:
@+/-250RPM

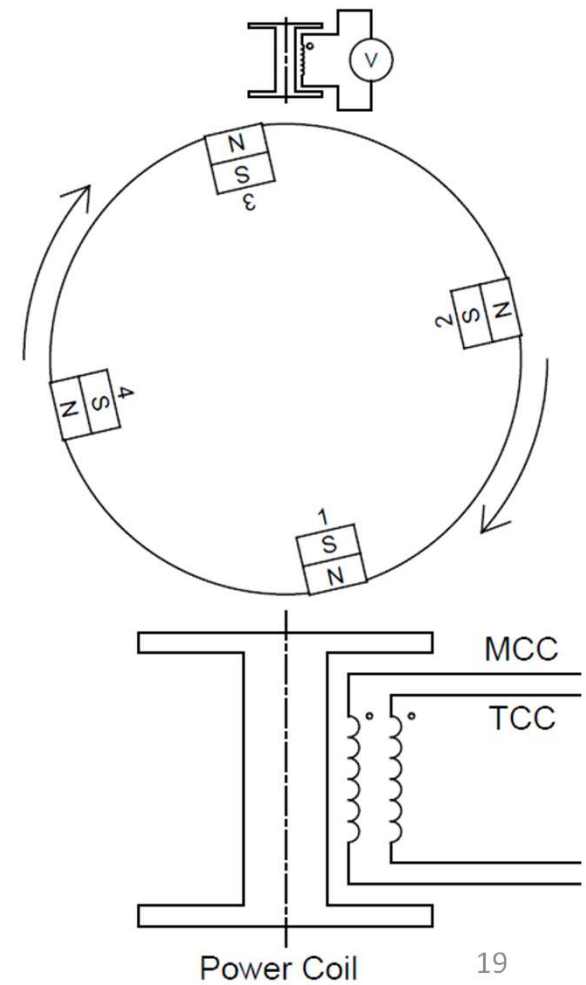

Appendix 4.3

Trigger Coil test

Proposal circuit for (trigger) coil MOSFET circuit

Note:

-Coil should be able to generate sufficient voltage to overcome the diode and still surpass the maximum gate threshold of the MOSFET

-Coil (and diodes) connections can be flipped around in case timing/magnetic field is reversed (like with the Hall sensor)

